

同济大学计算机系

计算机组成原理实验报告



学 号 2152809

姓 名 曾崇然

专 业 计算机科学与技术

授课老师 张冬冬老师

一、实验内容

学习了解除法器的原理，实现一个 32 位无符号除法器和一个 32 位带符号除法器

二、模块建模

32 位无符号除法器:

功能描述：将两个 32 位无符号数相除，得到一个 32 位商和 32 位余数。

verilog 代码:

```
module DIVU(
input [31:0]dividend,
input [31:0]divisor,
input start,
input clock,
input reset,
output [31:0]q,
output [31:0]r,
output reg busy
);
reg[4:0]count;
reg [31:0] reg_q;
reg [31:0] reg_r;
reg [31:0] reg_b;
reg r_sign;
wire [32:0] sub_add=r_sign?({reg_r,reg_q[31]}+{1'b0,reg_b}):({reg_r,reg_q[31]}-{1'b0,reg_b});
assign r = r_sign? reg_r + reg_b : reg_r;
assign q = reg_q;
always @ (posedge clock or posedge reset)
begin
    if(reset == 1)
    begin
        count <=5'b0;
        busy <= 0;
    end
    else
    begin
        if (start)
        begin
            reg_r <= 32'b0;
            r_sign <= 0;
            reg_q <= dividend;
            reg_b <= divisor;
            count <= 5'b0;
```

```

        busy <= 1'b1;
    end
    else if (busy)
    begin
        reg_r <= sub_add[31:0];
        r_sign <= sub_add[32];
        reg_q <= {reg_q[30:0],~sub_add[32]};
        count <= count +5'b1;
        if (count == 5'h1f)
            busy <= 0;
        end
    end
end
endmodule

```

32 位带符号除法器:

功能描述: 将两个 32 位带符号数相除, 得到带符号的 32 位商和 32 位余数

verilog 代码:

```

module DIV(
input [31:0] dividend,
input [31:0] divisor,
input start,
input clock,
input reset,
output [31:0] q,
output [31:0] r,
output reg busy
);
reg[4:0]count;
reg [31:0] reg_q;
reg [31:0] reg_r;
reg [31:0] reg_b;
reg r_sign;
reg sign_d,sign_r;
wire [31:0] mid_q;
wire [31:0] mid_r;
wire [32:0] sub_add=r_sign?({reg_r,reg_q[31]}+{1'b0,reg_b}):({reg_r,reg_q[31]}-{1'b0,reg_b});
assign mid_r = r_sign? reg_r + reg_b : reg_r;
assign mid_q = reg_q;
assign r=sign_d?-mid_r:mid_r;
assign q=(sign_d^sign_r)?-mid_q:mid_q;
always @ (posedge clock or posedge reset)
begin
    if(reset == 1)

```

```

begin
    count <= 5'b0;
    busy <= 0;
end
else
begin
    if (start)
    begin
        reg_r <= 32'b0;
        r_sign <= 0;
        if(dividend[31]==0)
            reg_q <= dividend;
        else
            reg_q <= -dividend;
        if(divisor[31]==0)
            reg_b <= divisor;
        else
            reg_b = -divisor;
        sign_d <= dividend[31];
        sign_r <= divisor[31];
        count <= 5'b0;
        busy <= 1'b1;
    end
    else if (busy)
    begin
        reg_r <= sub_add[31:0];
        r_sign <= sub_add[32];
        reg_q <= {reg_q[30:0], ~sub_add[32]};
        count <= count + 5'b1;
        if (count == 5'h1f)
        begin
            busy <= 0;
        end
    end
end
end
endmodule

```

三、测试模块建模

32 位无符号除法器:

```

module DIVU_tb();
reg [31:0] dividend;
reg [31:0] divisor;

```

```

wire start;
reg is_div;
reg clock;
reg reset;
wire [31:0] q;
wire [31:0] r;
wire busy;
assign start=is_div&~busy;
DIVU DIVU_inst(dividend,divisor,start,clock,reset,q,r,busy);
initial
begin
    clock=0;
    reset=1;
    is_div=0;
    dividend=524;
    divisor=13;
    #50 reset=0;
    #5 is_div=1;
    #20 is_div=0;
end
always
begin
    #10 clock=~clock;
end
endmodule

```

32 位带符号除法器:

```

module DIV_tb();
reg [31:0] dividend;
reg [31:0] divisor;
wire start;
reg is_div;
reg clock;
reg reset;
wire [31:0] q;
wire [31:0] r;
wire busy;
assign start=is_div&~busy;
DIV DIV_inst(dividend,divisor,start,clock,reset,q,r,busy);
initial
begin
    clock=0;
    reset=1;
    is_div=0;

```

```

dividend=-5;
divisor=-2;
#50 reset=0;
#5 is_div=1;
#20 is_div=0;
end
always
begin
    #10 clock=~clock;
end
endmodule

```

四、实验结果

32 位无符号除法器:



32 位带符号除法器:

